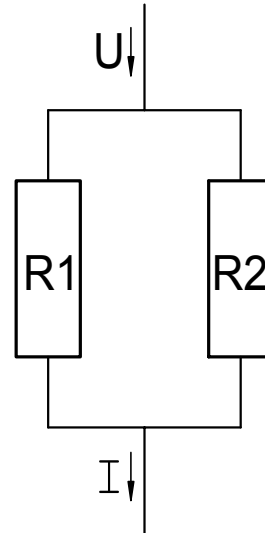


parallel:

$$R_{1,2} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$U = U_1 = U_2$$

$$I = I_1 + I_2$$



seriell:

$$R_{1,2} = R_1 + R_2$$

$$U = U_1 + U_2$$

$$I = I_1 = I_2$$

